



PHY335 Spring 2022 Lecture 5

Jan C. Bernauer

February 2022

# Universal amplifier gadget

So far, we only could reduce voltages. We need an **amplifier!**  
What would be the ultimate amplifier gadget?

# Universal amplifier gadget

So far, we only could reduce voltages. We need an **amplifier!**  
What would be the ultimate amplifier gadget?

- Arbitrary gain, positive and negative

# Universal amplifier gadget

So far, we only could reduce voltages. We need an **amplifier!**  
What would be the ultimate amplifier gadget?

- Arbitrary gain, positive and negative
- Linear



So far, we only could reduce voltages. We need an **amplifier!**  
What would be the ultimate amplifier gadget?

- Arbitrary gain, positive and negative
- Linear
- Infinite input impedance (so we don't load the source)

So far, we only could reduce voltages. We need an **amplifier!**  
What would be the ultimate amplifier gadget?


- Arbitrary gain, positive and negative
- Linear
- Infinite input impedance (so we don't load the source)
- Zero output impedance (so we can put arbitrary loads on it)

# Ideal op amp

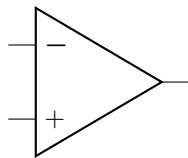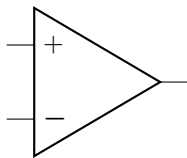


- One output (to the right)
- + is the non-inverting input
- - is the inverting input

# Ideal op amp

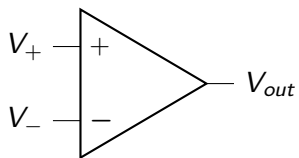




# Ideal op amp

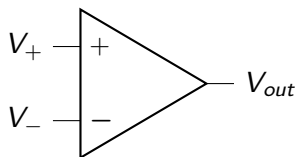

$$V_{out} = A \cdot (V_+ - V_-) = AV_D$$

# Ideal op amp

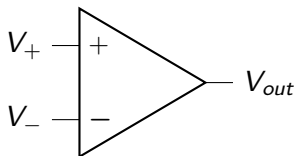


$$V_{out} = A \cdot (V_+ - V_-) = AV_D$$

For an ideal op amp,  $A = \infty$ . So for any any  $V_+ \neq V_-$ ,  $|V_{out}| = \infty$


Any system where a fraction of the output is fed back into the system is said to have feedback. Feedback is either

- **positive: the feedback increases the effective input**  
Mostly with catastrophic consequences.
- **negative: the feedback reduces the effective input**  
This is what we need now!  
(also improves linearity)

# Voltage follower

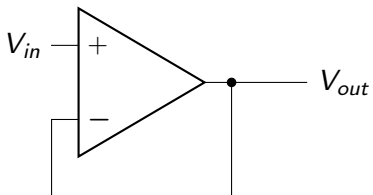


# Voltage follower

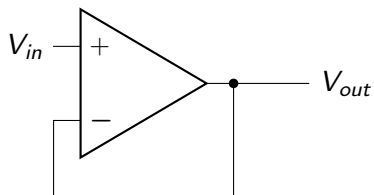

This is obviously negative feedback :)


# Voltage follower

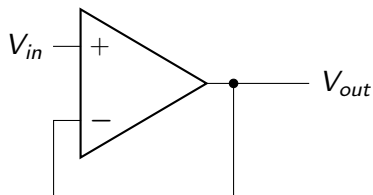

This is obviously negative feedback :)

- Let's assume at  $t=0$ ,  $V_{in} = 0$ ,  $V_{out} = 0$

# Voltage follower

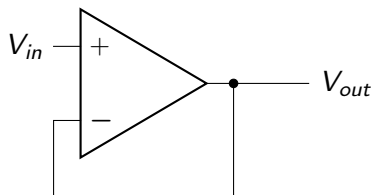

This is obviously negative feedback :)

- Let's assume at  $t=0$ ,  $V_{in} = 0$ ,  $V_{out} = 0$
- If  $V_{in}$  increases, the opamp sees a small voltage difference between its inputs:  $V_D = V_{in} - V_{out}$
- $V_{out}$  will increase until  $V_D$  is zero again

$$V_{out} = A(V_{in} - V_{out})$$



$$V_{out} = A(V_{in} - V_{out})$$

$$(A + 1)V_{out} = AV_{in}$$

$$V_{out} = A(V_{in} - V_{out})$$

$$(A + 1)V_{out} = AV_{in}$$

$$\frac{A + 1}{A} V_{out} = V_{in}$$

$$V_{out} = A(V_{in} - V_{out})$$

$$(A + 1)V_{out} = AV_{in}$$

$$\frac{A + 1}{A} V_{out} = V_{in}$$

For  $A \rightarrow \infty$

$$V_{out} = V_{in}$$

## But why?

No current flowing into the inputs. Output can source arbitrary currents.

That means:

- It appears as infinite resistance: the source of  $V_{in}$  is not loaded, i.e. not affected by connecting the voltage follower
- The output voltage is not affected by a load connected to the output

The voltage follower can be used as a buffer, separating a load from an input.

## Example for linearity improvement

Let's assume our real opamp is not linear, but still has a large amplification. For example, let's assume

$$V_{out} = 10^5 V_D \times \sqrt{V_D/1V}$$

## Example for linearity improvement

Let's assume our real opamp is not linear, but still has a large amplification. For example, let's assume

$$V_{out} = 10^5 V_D \times \sqrt{V_D/1V}$$

We could now build a  $\times 1$  amplifier by setting  $V_+ = V_{in}$ ,  $V_- = 0$ , and adding a  $1 : 10^5$  voltage divider. But then

$$V_{out} = V_{in} \times \sqrt{V_{in}/1V}$$

## Example for linearity improvement II

Instead, for a voltage follower with this horrible opamp, we would get:

$$V_{out} = 10^5(V_{in} - V_{out})\sqrt{(V_{in} - V_{out})/1V}$$

## Example for linearity improvement II

Instead, for a voltage follower with this horrible opamp, we would get:

$$V_{out} = 10^5(V_{in} - V_{out})\sqrt{(V_{in} - V_{out})/1V}$$

$$V_{out}^2 = 10^{10}(V_{in} - V_{out})^2(V_{in} - V_{out})/1V$$

$$10^{-10}V_{out}^2 1V = (V_{in} - V_{out})^3$$

$$V_{out} + (10^{-10}V_{out}^2 1V)^{1/3} = V_{in}$$



## Example for linearity improvement II

Instead, for a voltage follower with this horrible opamp, we would get:

$$V_{out} = 10^5(V_{in} - V_{out})\sqrt{(V_{in} - V_{out})/1V}$$

$$V_{out}^2 = 10^{10}(V_{in} - V_{out})^2(V_{in} - V_{out})/1V$$

$$10^{-10}V_{out}^2 1V = (V_{in} - V_{out})^3$$


$$V_{out} + (10^{-10}V_{out}^2 1V)^{1/3} = V_{in}$$

Seems pretty linear: 10V output would correspond to 10.002V input instead of  $\sim 4.644V$


# The Golden Rules

- There is no current flowing into the inputs
- In a working circuit with feedback,  $V_{out}$  is so that  $V_+ = V_-$

# Non-inverting amplifier

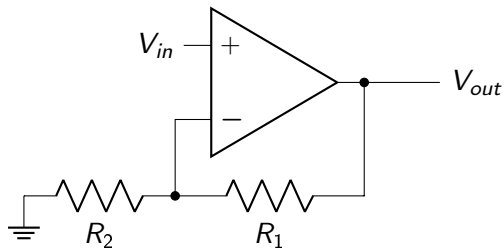

# Non-inverting amplifier

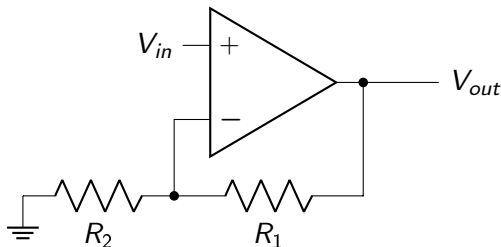


- $V_{in} = V_{+}$ ,  $R_2 \rightarrow V_{in} = V_{-}$
- There is no current into the inverting input. Unloaded voltage divider.

$$V_{-} = V_{out} \frac{R_2}{R_1 + R_2} = V_{in}$$


- So, voltage gain is

$$G_V = \frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_2}$$

# Inverting amplifier

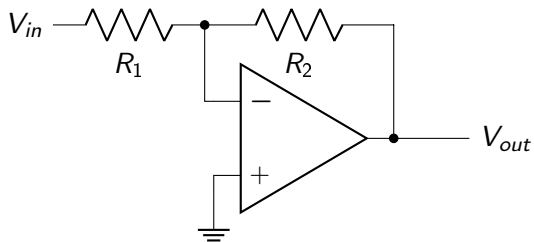

## Inverting amplifier

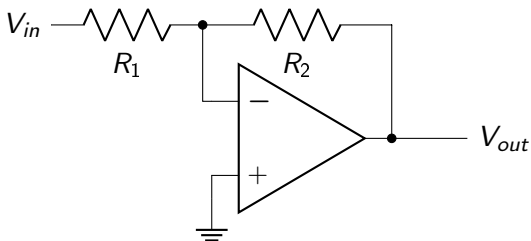

- $V_+ = 0V$ , so  $V_- = 0V$  (This is called a virtual ground.)
- No current into  $-$ , so

$$\frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} = 0$$


- Voltage gain:

$$G_V = -\frac{R_2}{R_1}$$


- However:

$$Z_{in} = R_1$$

# Non-working inverting amplifier

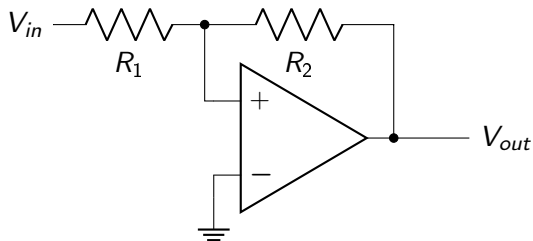


## Non-working inverting amplifier

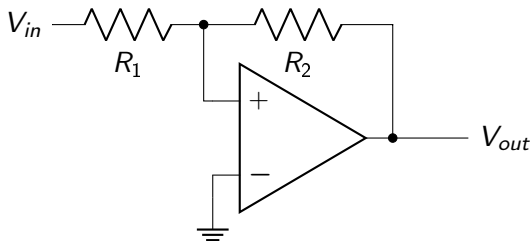


This circuit does not have negative feedback.  
Golden rules do not apply!



## Voltage adder

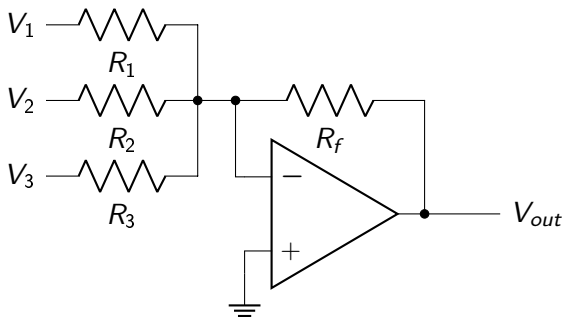

## Voltage adder

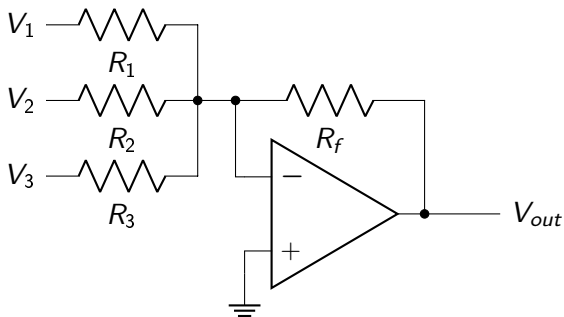

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_{out}}{R_f} = 0$$

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

If  $R_f = R_1 = R_2 = R_3$ :

$$V_{out} = -(V_1 + V_2 + V_3)$$

# Some notes about real opamps

## Real op amps

- have finite amplification
- have amplification which depends on frequency

# Some notes about real opamps

## Real op amps

- have finite amplification
- have amplification which depends on frequency
- need power

# Some notes about real opamps

## Real op amps

- have finite amplification
- have amplification which depends on frequency
- need power
- can actually not drive that much current


## Some notes about real opamps

### Real op amps

- have finite amplification
- have amplification which depends on frequency
- need power
- can actually not drive that much current
- restrictions on input
- restrictions on output (except rail-to-rail)
- take time to come out of overdrive (output at the min/max)
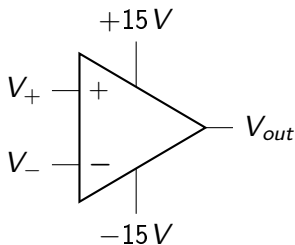
# Power supply


Most often need a split supply:  $\pm xV$ , often  $\pm 15V$  (exception: single supply op amps). Circuit diagram:



In circuit diagrams, the positive rail is often named  $V_{CC}$ , the negative  $V_{EE}$


**DANGER:** Sometimes, they are also named  $V_+$  and  $V_-$

# Differential Amplifier

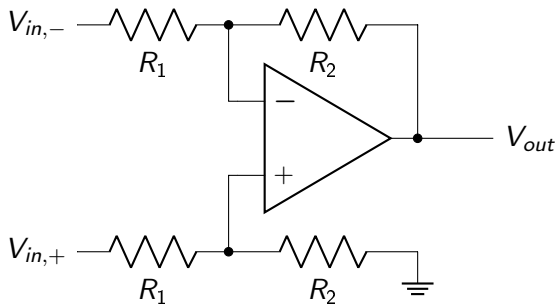




# Differential Amplifier

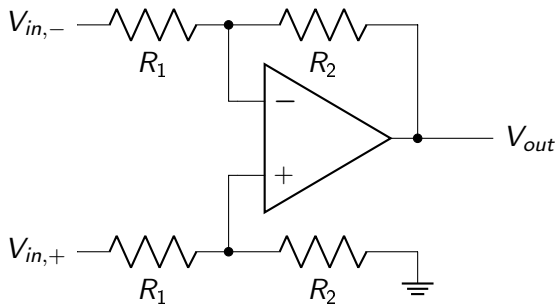

$$V_+ = V_{in,+} \frac{R_2}{R_1 + R_2}$$


# Differential Amplifier

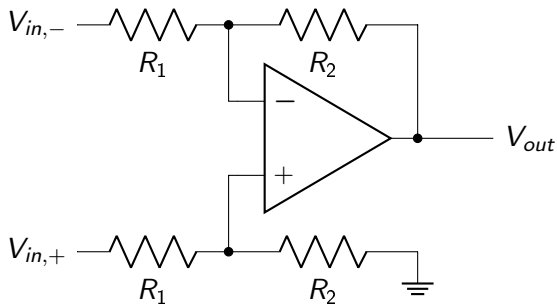

$$V_+ = V_{in,+} \frac{R_2}{R_1 + R_2}$$

$$V_- = (V_{in,-} - V_{out}) \frac{R_2}{R_1 + R_2} + V_{out}$$

# Differential Amplifier

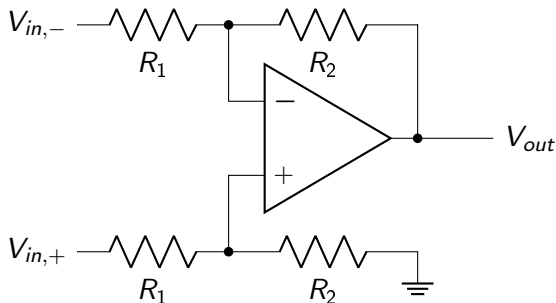

$$V_+ = V_{in,+} \frac{R_2}{R_1 + R_2}$$

$$V_- = (V_{in,-} - V_{out}) \frac{R_2}{R_1 + R_2} + V_{out}$$

$$V_+ = V_-$$

$$(V_{in,-} - V_{out}) \frac{R_2}{R_1 + R_2} + V_{out} = V_{in,+} \frac{R_2}{R_1 + R_2}$$

$$(V_{in,-} - V_{out}) \frac{R_2}{R_1 + R_2} + V_{out} = V_{in,+} \frac{R_2}{R_1 + R_2}$$

$$(V_{in,-} - V_{out}) + \frac{R_2 + R_1}{R_2} V_{out} = V_{in,+}$$

$$(V_{in,-} - V_{out}) \frac{R_2}{R_1 + R_2} + V_{out} = V_{in,+} \frac{R_2}{R_1 + R_2}$$

$$(V_{in,-} - V_{out}) + \frac{R_2 + R_1}{R_2} V_{out} = V_{in,+}$$

$$\left( \frac{R_2 + R_1}{R_2} - 1 \right) V_{out} = V_{in,+} - V_{in,-}$$


$$(V_{in,-} - V_{out}) \frac{R_2}{R_1 + R_2} + V_{out} = V_{in,+} \frac{R_2}{R_1 + R_2}$$

$$(V_{in,-} - V_{out}) + \frac{R_2 + R_1}{R_2} V_{out} = V_{in,+}$$

$$\left(\frac{R_2 + R_1}{R_2} - 1\right) V_{out} = V_{in,+} - V_{in,-}$$


$$V_{out} = \frac{R_2}{R_1} (V_{in,+} - V_{in,-})$$
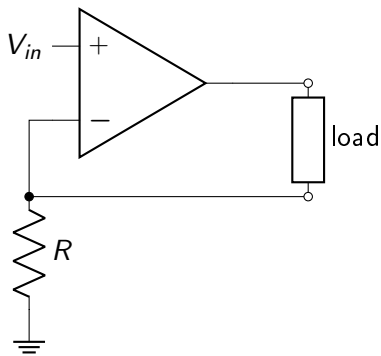
# Opamp as a (voltage controlled) current source





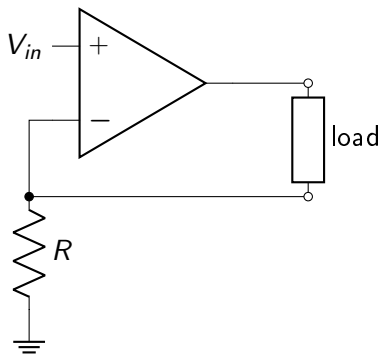
## Opamp as a (voltage controlled) current source



GRs:  $V_- = V_+ = V_{in}$

$$I_{load} = \frac{V_-}{R} = \frac{V_{in}}{R}$$
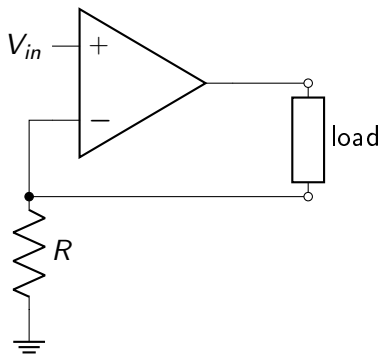
## Opamp as a (voltage controlled) current source




GRs:  $V_- = V_+ = V_{in}$


$$I_{load} = \frac{V_-}{R} = \frac{V_{in}}{R}$$

Not ideal: Load does not return to ground.

# Integrator

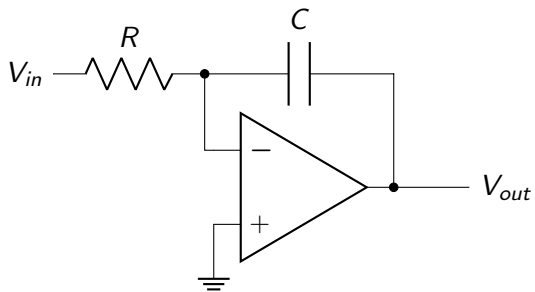


# Integrator

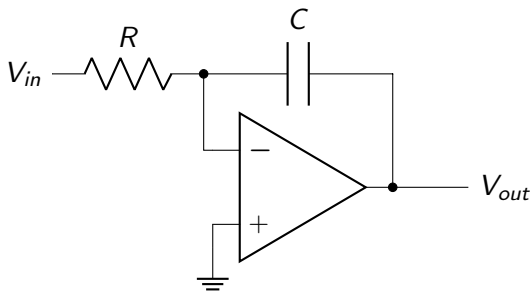

$$\frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$


# Integrator

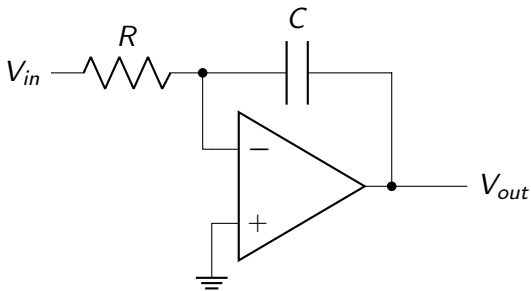

$$\frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$

$$V_{out}(t) = \frac{1}{RC} \int V_{in}(t) + \text{const.}$$

# Integrator

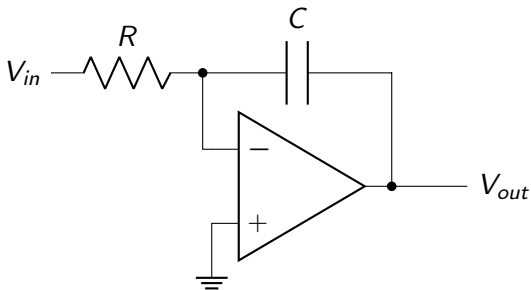


$$\frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$


$$V_{out}(t) = \frac{1}{RC} \int V_{in}(t) + \text{const.}$$

Problem: No feedback for DC

# Integrator

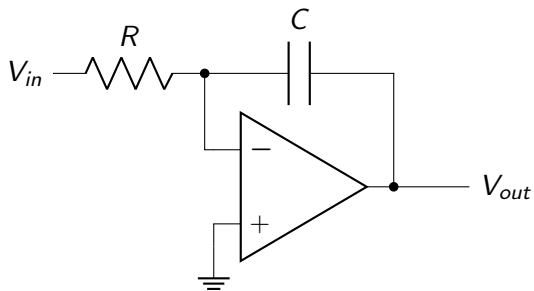


# Integrator

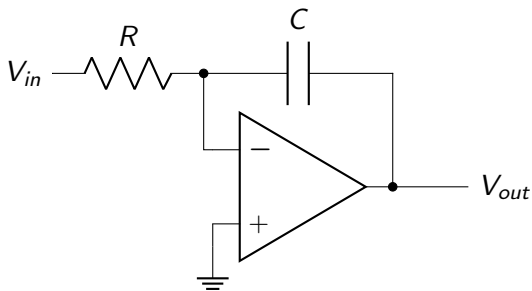

$$\frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$




# Integrator

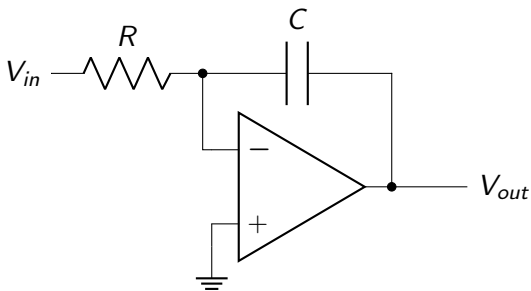

$$\frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$

$$V_{out}(t) = -\frac{1}{RC} \int V_{in}(t) + \text{const.}$$

# Integrator

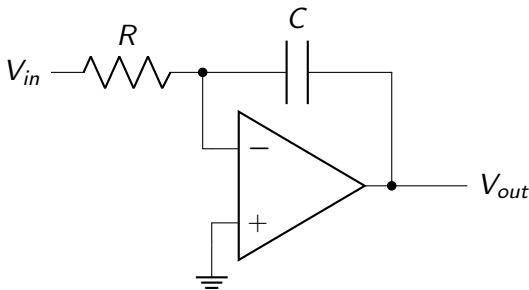

$$\frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$

$$V_{out}(t) = -\frac{1}{RC} \int V_{in}(t) + \text{const.}$$

Problem: No feedback for DC. Need to "zero" by shorting out C from time to time.

Let's look at the performance of a real op amp.


- There is some small input current,  $I_B$ .
- If  $V_{in}$  is not connected, this will produce a voltage drift of  $\frac{dV}{dt} = \frac{I_B}{C}$ .
- For the TL082,  $I_B = 50\text{pA}$
- Let's say, for 10nF, we see  $\frac{dV_{out}}{dt} = 5\text{mV/s}$

Let's say  $V_{in}$  is actually connected to ground.

- The op amp actually has some input voltage offset,  $V_{OS}$  (in the sense that  $V_D = V_+ - V_- - V_{OS}$ )
- In other words, with  $V_- = 0V$ ,  $V_+ = V_{OS}$
- This will produce a current through  $R$
- For the TL082,  $V_{OS}$  is 5mV.
- With  $R = 1M\Omega$ , i.e. 5 nA
- That's a 100 times worse than the error from  $I_B$

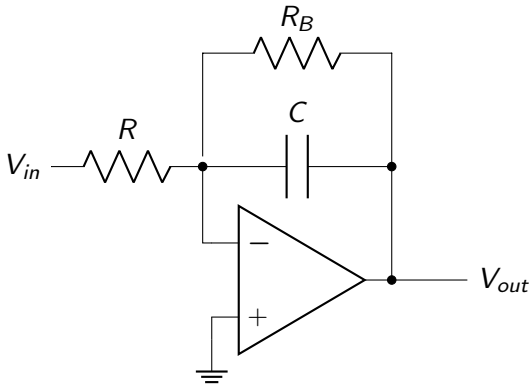
## Combating drift with a T-network

We can also add a (large) resistor parallel to C to give DC negative feedback.



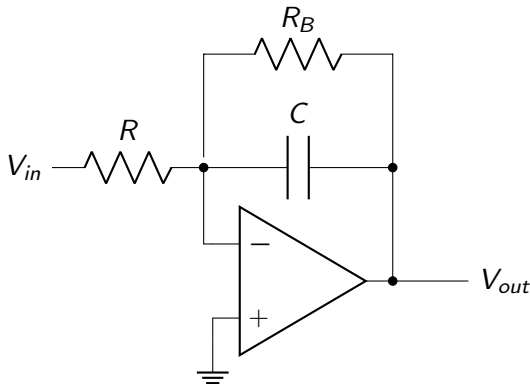
## Combating drift with a T-network

We can also add a (large) resistor parallel to  $C$  to give DC negative feedback.




We want to make  $R_B$  very, very large. These resistors are hard to come by and have bad parasitic parameters (mainly capacitance)

## Combating drift with a T-network II

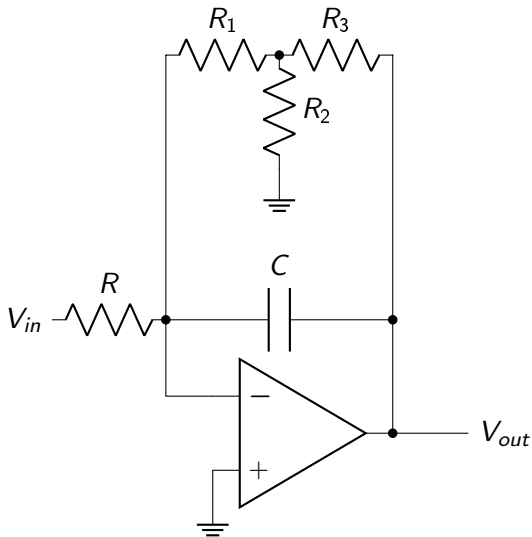


## How does that work?

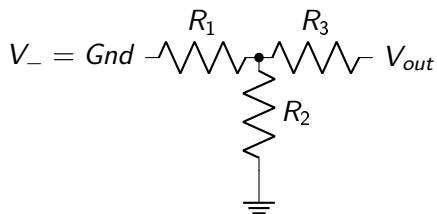

- $R_1$  and  $R_2$  both connect the T-node to (virtual) ground.




## How does that work?

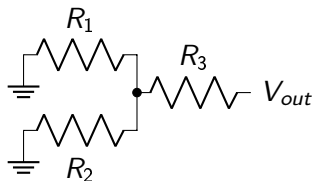

- $R_1$  and  $R_2$  both connect the T-node to (virtual) ground.
- $R_2 \ll R_1 = R_3$ , which mean  $R_3 + R_2 \approx R_3$  and  $R_1 \parallel R_2 \approx R_2$


## How does that work?

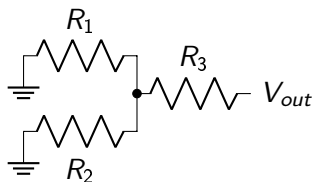


- $R_1$  and  $R_2$  both connect the T-node to (virtual) ground.
- $R_2 \ll R_1 = R_3$ , which mean  $R_3 + R_2 \approx R_3$  and  $R_1 \parallel R_2 \approx R_2$
- So the voltage at the T-node is given by a voltage divider:

$$V_{T-node} = V_{out} \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_3} = V_{out} \frac{R_2}{R_3}$$

On the other hand

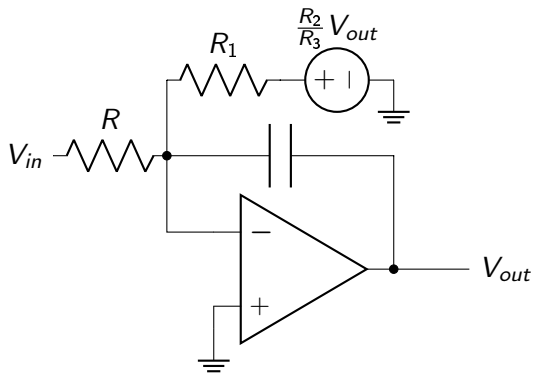


## On the other hand

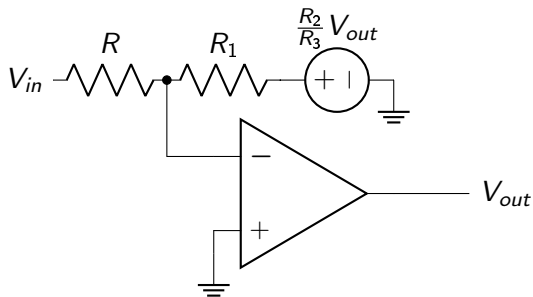

At DC, i.e.  $\omega = 0$ , we can ignore the capacitor.

## On the other hand

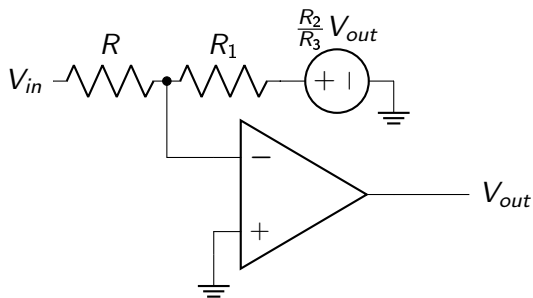


At DC, i.e.  $\omega = 0$ , we can ignore the capacitor.

$$\frac{V_{in}}{R} = -\frac{V_{T-node}}{R_1} = V_{out} \frac{R_2}{R_1 R_3}$$


The T-Network acts like a large resistor of the value

$$R_T = \frac{R_1 R_3}{R_2}$$

# Differentiator

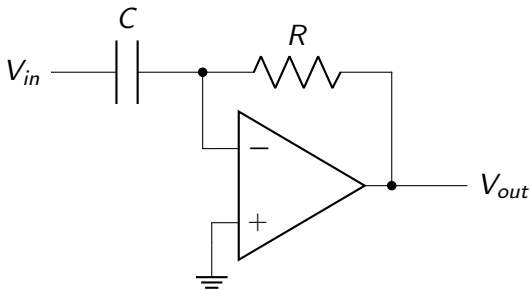


# Differentiator

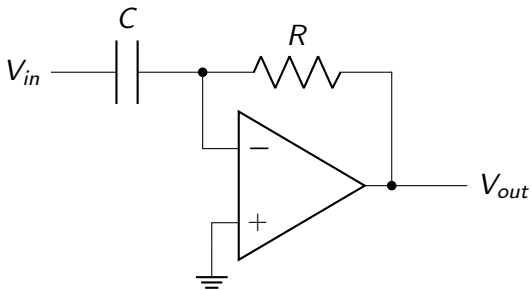

$$C \frac{dV_{in}}{dt} = I = -\frac{V_{out}}{R}$$

# Differentiator

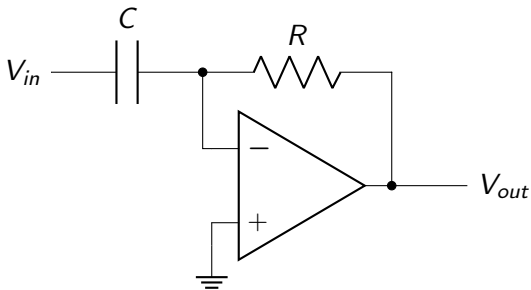

$$C \frac{dV_{in}}{dt} = I = -\frac{V_{out}}{R}$$

$$V_{out} = -RC \frac{dV_{in}}{dt}$$



The output of an opamp can only change at a certain, type dependent, maximal rate. This is the so called **slew rate SR**.


- The slew rate is visible for example if the output should be a square wave, where the voltage level changes are not instantaneous.
- Or as a distortion in a waveform. For a sine wave,

$$\frac{dV}{dt} = V_0 \omega \cos \omega t$$

so the frequency at which distortions appear gives the slew rate as  $SR = 2\pi V_0 f$

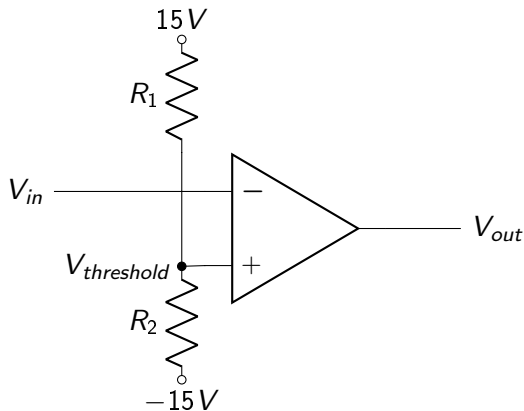
## Opamps as comparators

Let's look at a case when no feedback is applied:




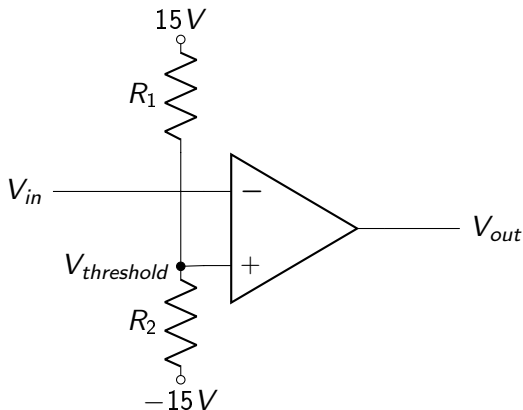
## Opamps as comparators

Let's look at a case when no feedback is applied:




For  $V_{in} \neq V_{Threshold}$ , the output will saturate at its minimum or maximum. Optimized opamps for this purpose exist, they are called **comparators**. Simplest form of an analog to digital converter!

# Unstable transition

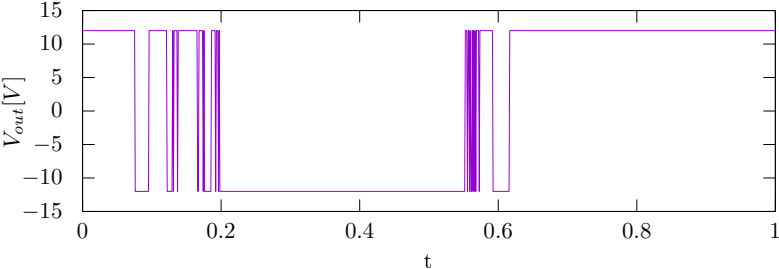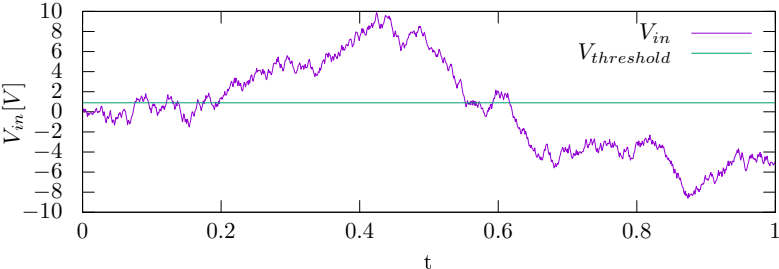


# Schmitt-Trigger

Adding **positive** feedback can help:

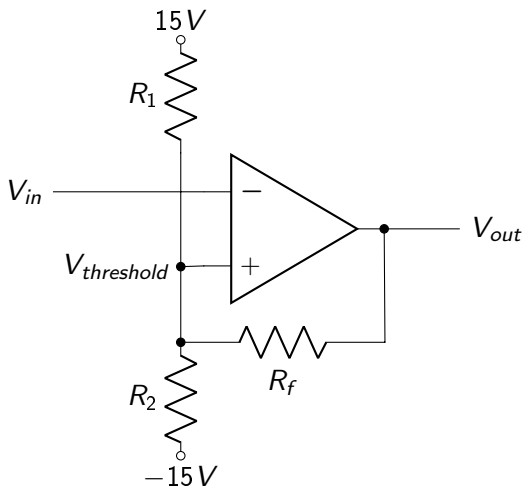



# Schmitt-Trigger

Adding **positive** feedback can help:

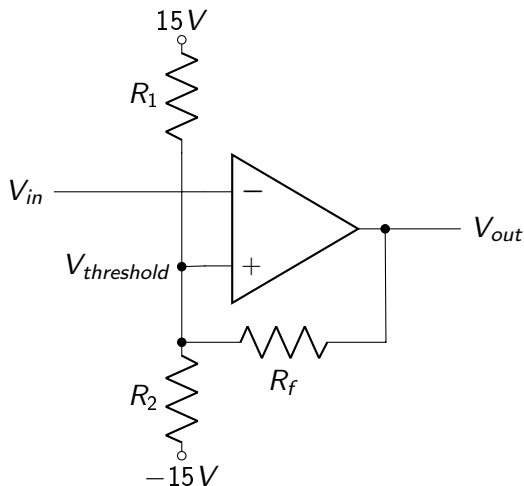

The positive feedback adds **hysteresis**!

# Schmitt-Trigger II

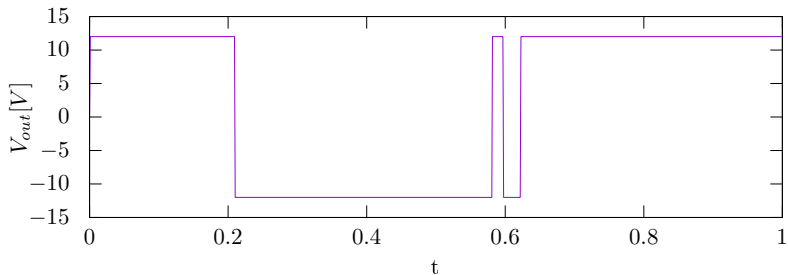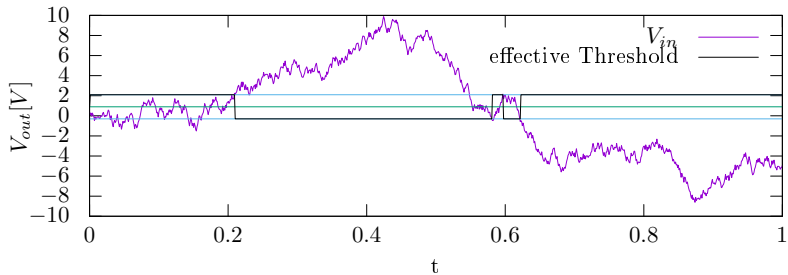

## Unit 5 comments

Unit 5, question 2 asks you to build a voltage divider with a potentiometer and two resistors to set a voltage from  $\pm 5V$  using a supply of  $\pm 15V$ .



- There are  $30V$  across 3 resistors of the same size.  $\rightarrow$  each resistor drops the same voltage,  $10V$



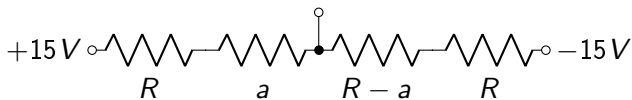
## Unit 5 comments


Unit 5, question 2 asks you to build a voltage divider with a potentiometer and two resistors to set a voltage from  $\pm 5V$  using a supply of  $\pm 15V$ .



- There are  $30V$  across 3 resistors of the same size.  $\rightarrow$  each resistor drops the same voltage,  $10V$
- One can think of the potentiometer as two resistances which sum up to  $10k$ :



## How stiff is this source?

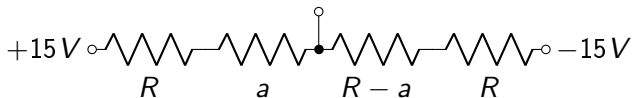


Thevenin equivalent  $R$ :

$$R_{Th} = (R + a) \parallel (R + R - a) = \frac{1}{\frac{1}{R+a} + \frac{1}{2R-a}} = \frac{2R^2 + Ra - a^2}{3R}$$

Minimum:  $a = 0$  or  $a = R$ ,  $R_{Th} = \frac{2}{3}R$ .

Maximum:  $a = R/2$ ,  $R_{th} = \frac{3}{4}R$

## How stiff is this source?

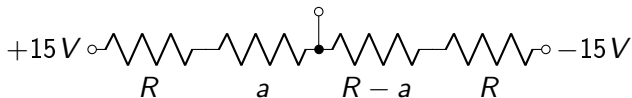

Thevenin equivalent R:

$$R_{Th} = (R + a) \parallel (R + R - a) = \frac{1}{\frac{1}{R+a} + \frac{1}{2R-a}} = \frac{2R^2 + Ra - a^2}{3R}$$

Minimum:  $a = 0$  or  $a = R$ ,  $R_{Th} = \frac{2}{3}R$ .

Maximum:  $a = R/2$ ,  $R_{th} = \frac{3}{4}R$

Relative change:  $\approx \pm 6\%$

## Why not directly to $\pm 5V$ ?



Now,  $R_{Th}$  between 0 and  $R/4$ . That's  $\pm 100\%$