



PHY335 Spring 2022 Lecture 6



Jan C. Bernauer

March 2022


Generally: Three poles!

- BJT: Bipolar (junction) transistors: npn / pnp
A current is controlled by a different current
- FET: Field effect transistors: n-channel / p-channel, (JFET, MOSFET etc.)
A current is controlled by a voltage

BJT: npn / pnp

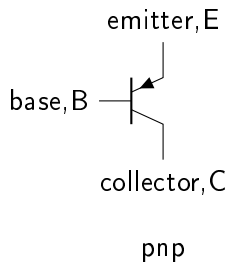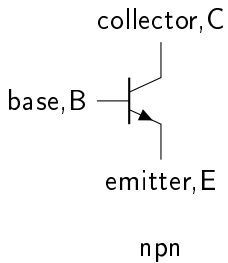


Nomenclature

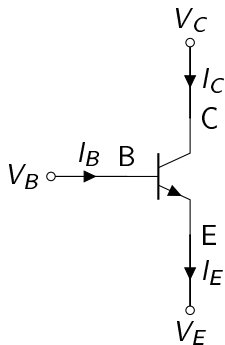


We are interested in **voltage differences** across the transistor:

- $V_{BE} = V_B - V_E$
- $V_{CE} = V_C - V_E$
- $V_{CB} = V_C - V_B$

Band diagram without voltages

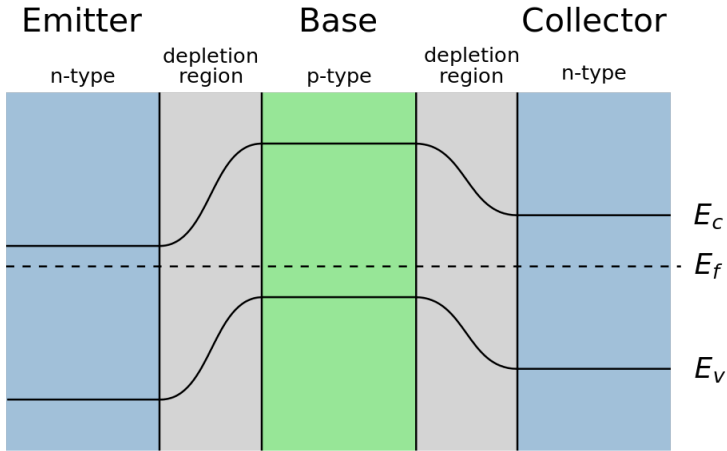


Band diagram in normal mode

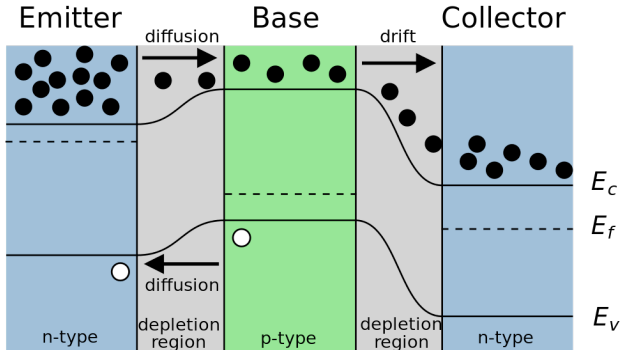

- The BE levels are shifted so that electrons (majority carriers in n, minority in p) can travel into the base.
- At the BC side, the field from the reverse bias drifts the electrons out.
- The density gradient across the thin base drives electrons across it via diffusion

Operation modes

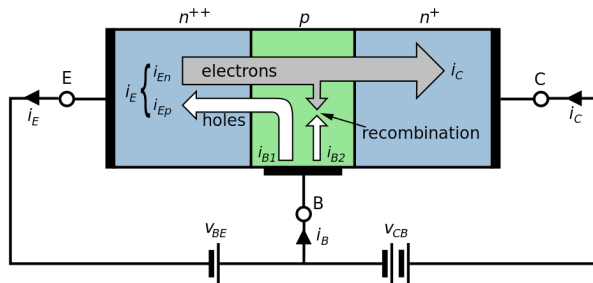

- Active: Base-emitter is forward biased ($V_{BE} > 0$), base-collector is reverse biased $V_{CB} > 0$. $i_C = \beta I_B$
- Reverse-active: Switch roles of C and E. Rarely used
- Saturation: $V_{BE} > 0$, $V_{CB} < 0$: maximum current
- Cut-off: $V_{BE} < 0$, $V_{CB} > 0$, both diodes in reverse, minimal current

Transistor rules for the "current model"

- Polarity: $V_{CE} > 0$

Transistor rules for the "current model"

- Polarity: $V_{CE} > 0$
- Junctions: The base-emitter and base-collector behave like diodes. (But collector-emitter current does not!)

Transistor rules for the "current model"

- Polarity: $V_{CE} > 0$
- Junctions: The base-emitter and base-collector behave like diodes. (But collector-emitter current does not!)
- Maximum ratings: If you are outside, the magic smoke escapes.

Transistor rules for the "current model"

- Polarity: $V_{CE} > 0$
- Junctions: The base-emitter and base-collector behave like diodes. (But collector-emitter current does not!)
- Maximum ratings: If you are outside, the magic smoke escapes.
- Then: Current amplifier: $I_C = h_{FE} I_B = \beta I_B$

β is a bad parameter: It can differ significantly for different specimen of the same type. (See datasheet)

$$V_{BE} \approx 0.6V$$


Or:

$$V_B = V_E + 0.6V$$

We want a constant current through a load, independent of the load impedance.


BJT current source

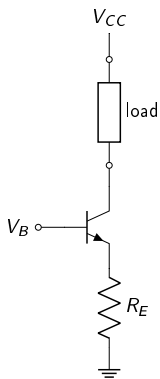We want a constant current through a load, independent of the load impedance.



BJT current source

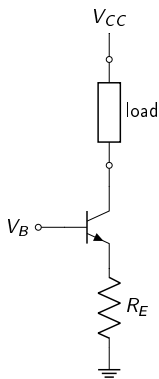
We want a constant current through a load, independent of the load impedance.



- $V_E = V_B - 0.6V$

BJT current source

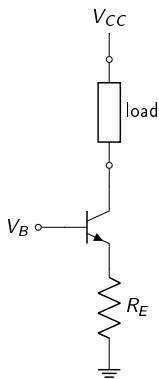
We want a constant current through a load, independent of the load impedance.



- $V_E = V_B - 0.6V$
- $I_E = V_E / R_E$

BJT current source

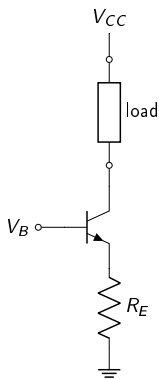
We want a constant current through a load, independent of the load impedance.



- $V_E = V_B - 0.6V$
- $I_E = V_E / R_E$
- $I_{load} = I_C = I_E - I_B = I_E(1 - 1/(\beta + 1)) \approx I_E$


BJT current source

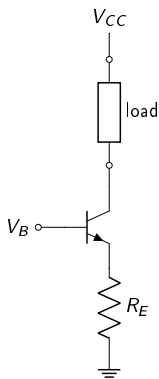We want a constant current through a load, independent of the load impedance.




- $V_E = V_B - 0.6V$
- $I_E = V_E/R_E$
- $I_{load} = I_C = I_E - I_B = I_E(1 - 1/(\beta + 1)) \approx I_E$
- So: $I_{load} = \frac{V_B - 0.6V}{R_E}$
- True as long as $V_E + 0.2V < V_C < V_{CC}$

Emitter follower

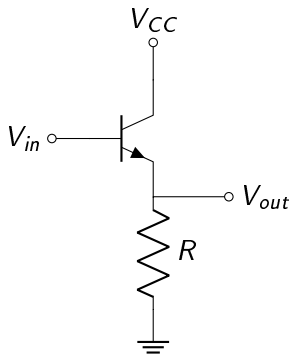


Emitter follower

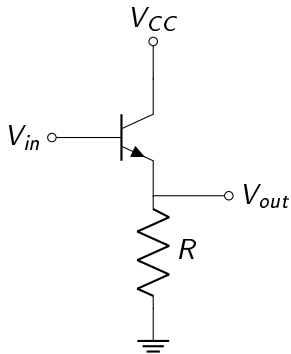


- $V_{out} = V_{in} - 0.6V$
- Feedback: "Signal" to transistor is $V_{BE} = V_B - V_E = V_{in} - V_{out}$

Input impedance

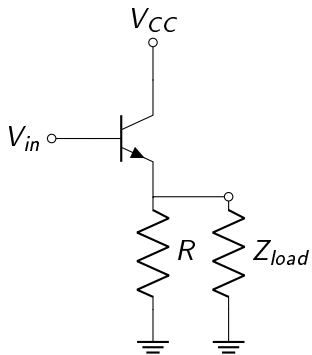


Input impedance

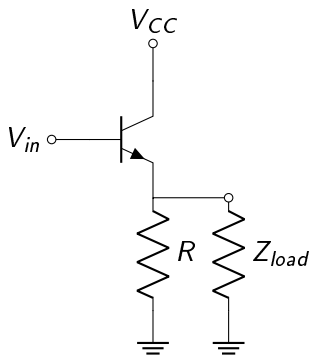

$$\Delta V_B = \Delta V_E \longrightarrow \Delta I_E = \frac{\Delta V_E}{R \parallel Z_{load}} = \frac{\Delta V_B}{R \parallel Z_{load}}$$


Input impedance

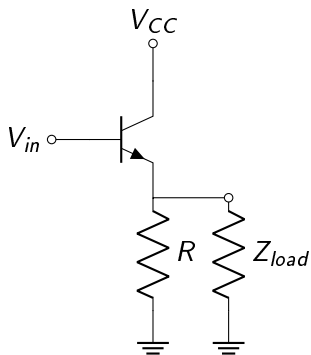

$$\Delta V_B = \Delta V_E \longrightarrow \Delta I_E = \frac{\Delta V_E}{R \parallel Z_{load}} = \frac{\Delta V_B}{R \parallel Z_{load}}$$

$$\Delta I_B = \frac{\Delta I_E}{\beta + 1}$$

Input impedance

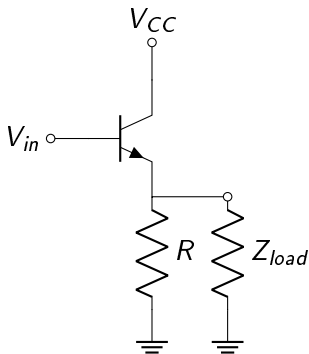


$$\Delta V_B = \Delta V_E \longrightarrow \Delta I_E = \frac{\Delta V_E}{R \parallel Z_{load}} = \frac{\Delta V_B}{R \parallel Z_{load}}$$


$$\Delta I_B = \frac{\Delta I_E}{\beta + 1}$$

$$r_{in} = \frac{\Delta V_B}{\Delta I_B} = (\beta + 1)(R \parallel Z_{load}) = \beta(R \parallel Z_{load})$$

Output impedance

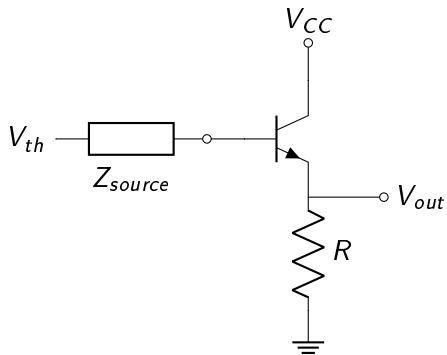


Output impedance

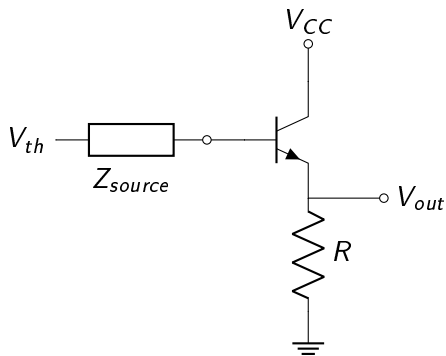


$$r_{out} = \frac{\Delta V_E}{\Delta I_E} = \frac{\Delta V_B}{(\beta+1)\Delta I_B} = Z_{source} \frac{1}{\beta+1} = Z_{source} / \beta$$

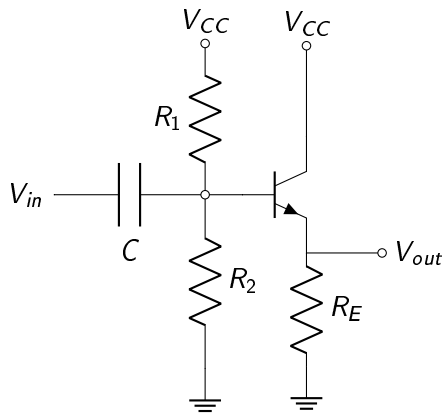AC coupled emitter follower, working point




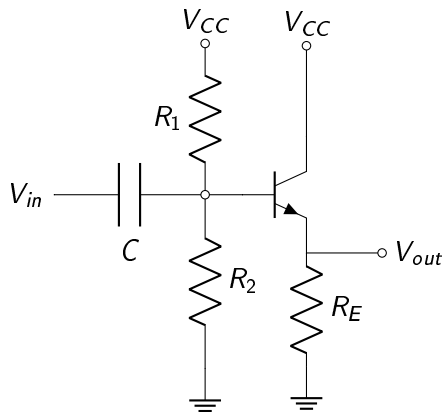AC coupled emitter follower, working point




- We want the working point for $V_{out} = V_{CC}/2$ if we don't have an input, and we need to pick a bias current I_{bias} . This gives $R_E = V_{CC}/(2I_{bias})$

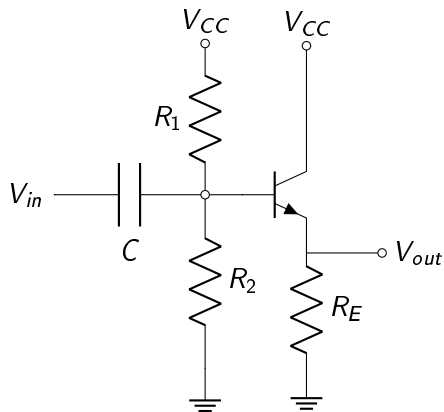AC coupled emitter follower, working point




- We want the working point for $V_{out} = V_{CC}/2$ if we don't have an input, and we need to pick a bias current I_{bias} . This gives $R_E = V_{CC}/(2I_{bias})$
- We need to pick the voltage divider ratio (R_1, R_2) so that $V_B = V_{CC}/2 + 0.6V$

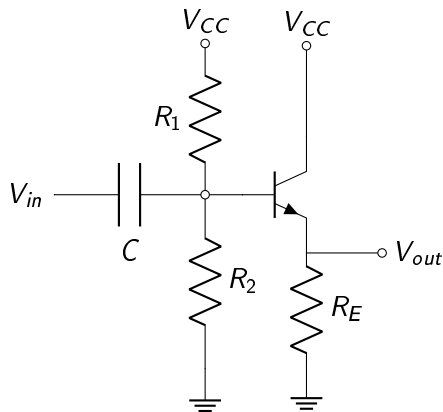AC coupled emitter follower, working point



- We want the working point for $V_{out} = V_{CC}/2$ if we don't have an input, and we need to pick a bias current I_{bias} . This gives $R_E = V_{CC}/(2I_{bias})$
- We need to pick the voltage divider ratio (R_1, R_2) so that $V_B = V_{CC}/2 + 0.6V$
- We want $R_{1,2}$ large (to not load the source). But the divider is loaded by input impedance (see above). So, $R_1 \parallel R_2 < \beta R_E$


Common emitter amplifier

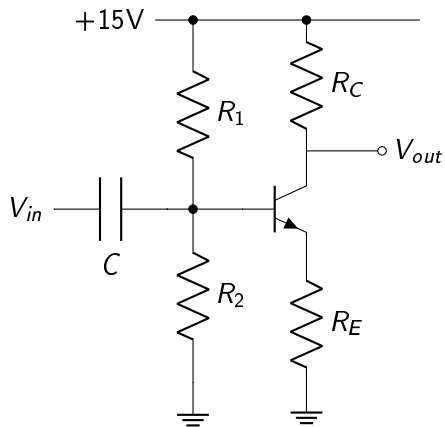

We are interested in changes from the working point

- Assume frequency is large enough


Common emitter amplifier

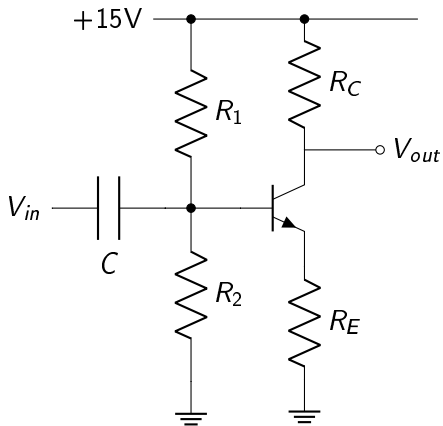

We are interested in changes from the working point

- Assume frequency is large enough
- $\Delta V_{in} = \Delta V_E \rightarrow v_{in} = v_E$


Common emitter amplifier

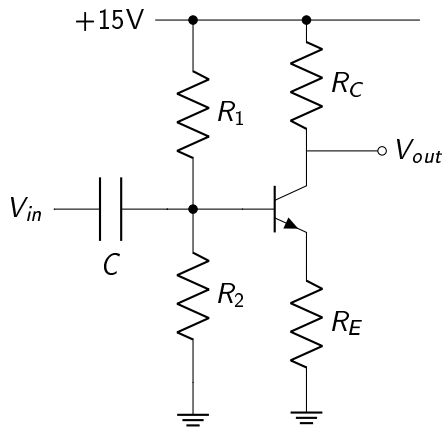

We are interested in changes from the working point

- Assume frequency is large enough
- $\Delta V_{in} = \Delta V_E \rightarrow v_{in} = v_E$
- $i_E = v_E / R_E$


Common emitter amplifier

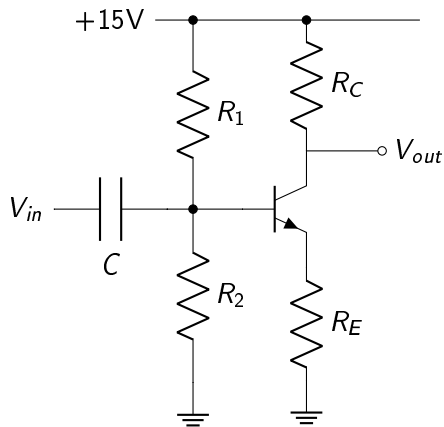

We are interested in changes from the working point

- Assume frequency is large enough
- $\Delta V_{in} = \Delta V_E \rightarrow v_{in} = v_E$
- $i_E = v_E / R_E$
- $i_C = \beta i_B = \beta \frac{i_E}{\beta + 1} \approx i_E$

Common emitter amplifier

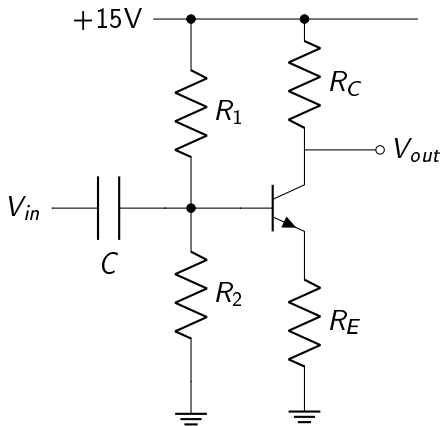

We are interested in changes from the working point

- Assume frequency is large enough
- $\Delta V_{in} = \Delta V_E \rightarrow v_{in} = v_E$
- $i_E = v_E / R_E$
- $i_C = \beta i_B = \beta \frac{i_E}{\beta + 1} \approx i_E$
- $v_{out} = v_C = -R_C i_C = -\frac{R_C}{R_E} v_{in}$

- Input: Looking into the input (ignore the C), we see $R_1 \parallel R_2 \parallel \beta R_E$
 - Together with the C, this gives a high-pass filter....

- Input: Looking into the input (ignore the C), we see $R_1 \parallel R_2 \parallel \beta R_E$
 - Together with the C, this gives a high-pass filter....
- Output: Without the R_C , this looks like a current source (see above)
 - Current sources have (ideally infinite) large resistances, so R_C dominates and is the output resistance

- Input: Looking into the input (ignore the C), we see $R_1 \parallel R_2 \parallel \beta R_E$
 - Together with the C, this gives a high-pass filter....
- Output: Without the R_C , this looks like a current source (see above)
 - Current sources have (ideally infinite) large resistances, so R_C dominates and is the output resistance
- This means that R_C is limited by what ever we want to drive, and large amplifications need then very small R_E . **How small can we make it?**

No emitter resistor: Ebers-Moll equation

What happens if we omit the emitter resistor?

- We can't assume $V_B = V_E + 0.7V$ any more

No emitter resistor: Ebers-Moll equation

What happens if we omit the emitter resistor?

- We can't assume $V_B = V_E + 0.7V$ any more
- Use diode equation: $I_E = I_S(T)(e^{\frac{eV_{BE}}{k_B T}} - 1)$

What happens if we omit the emitter resistor?

- We can't assume $V_B = V_E + 0.7V$ any more
- Use diode equation: $I_E = I_S(T)(e^{\frac{eV_{BE}}{k_B T}} - 1)$
- I.e.: $V_{BE} = \frac{k_B T}{e} \ln\left(\frac{I_E}{I_S(T)} + 1\right)$

What happens if we omit the emitter resistor?

- We can't assume $V_B = V_E + 0.7V$ any more
- Use diode equation: $I_E = I_S(T)(e^{\frac{eV_{BE}}{k_B T}} - 1)$
- I.e.: $V_{BE} = \frac{k_B T}{e} \ln\left(\frac{I_E}{I_S(T)} + 1\right)$
- (As usual, we can mostly neglect the 1)

No emitter resistor: Ebers-Moll equation

What happens if we omit the emitter resistor?

- We can't assume $V_B = V_E + 0.7V$ any more
- Use diode equation: $I_E = I_S(T)(e^{\frac{eV_{BE}}{k_B T}} - 1)$
- I.e.: $V_{BE} = \frac{k_B T}{e} \ln\left(\frac{I_E}{I_S(T)} + 1\right)$
- (As usual, we can mostly neglect the 1)
- A constant ΔV_{BE} gives a constant ratio $\frac{I_{E,2}}{I_{E,1}} = e^{\frac{e\Delta V_{BE}}{k_B T}}$

- $V_{BE} = \frac{k_B T}{e} \ln \left(\frac{I_E}{I_S(T)} + 1 \right)$

A closer look: r_E

- $V_{BE} = \frac{k_B T}{e} \ln \left(\frac{I_E}{I_S(T)} + 1 \right)$
- Linearize! We can find a small signal effective resistance:
 - $r = \frac{dV}{dI}$
 - In our case: $\frac{dV_{BE}}{dI_E} \approx \frac{k_B T}{eI_E} \approx \frac{25mV}{I_E}$


A closer look: r_E

- $V_{BE} = \frac{k_B T}{e} \ln \left(\frac{I_E}{I_S(T)} + 1 \right)$
- Linearize! We can find a small signal effective resistance:
 - $r = \frac{dV}{dI}$
 - In our case: $\frac{dV_{BE}}{dI_E} \approx \frac{k_B T}{e I_E} \approx \frac{25mV}{I_E}$
- This looks like an additional, **intrinsic resistance on the emitter pole**
- This limits the maximum amplification for the common emitter amplifier!

There is an additional problem with small R_E :


- Either the quiescent current is large \Leftrightarrow Power dissipation
- Or V_E is small \Leftrightarrow Large temperature drifts, since
$$\frac{dV_{BE}}{dT} \approx -2.1mV/^{\circ}C$$

Bypassing R_E

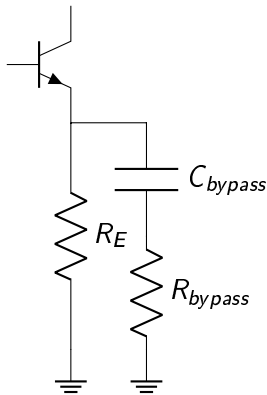


- For the working point, at DC, a normal size R_E gives good temperature stability
- For a signal of relevant frequency, the C_{bypass} has small impedance. Then, the emitter resistance is $R_E \parallel R_{bypass}$, which can be very small

Common-base amplifier

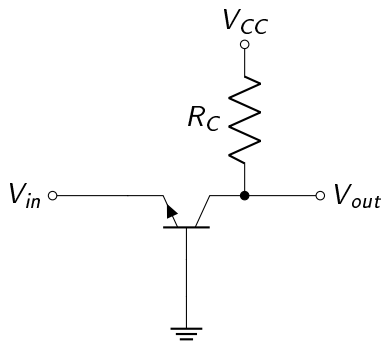

- $V_{in} < 0$
- Input impedance is very small:
 r_E

Common-base amplifier

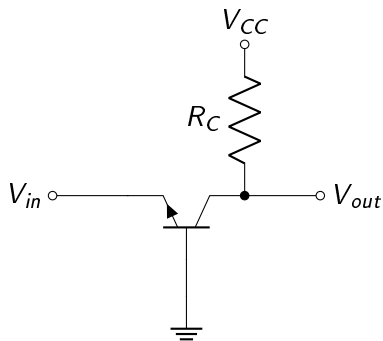

- $V_{in} < 0$
- Input impedance is very small: r_E
- This is good for current source-type of signals.
 - Many detectors are current sources, with some internal capacity.
 - Using a simple resistor to convert to voltage makes it slow
 - Transistor "hides" resistance, small $\tau = RC$

For PNP, reverse all polarities. Done.

Because now the current is carried via holes instead of electrons, they typically perform slightly worse.

Field Effect Transistors

BJTs control the current flow (CE) via the base current. Field Effect transistors control the flow via the presence of an **electric field**. You have to apply a voltage, but (essentially) no current flows.

BJTs control the current flow (CE) via the base current. Field Effect transistors control the flow via the presence of an **electric field**. You have to apply a voltage, but (essentially) no current flows.

Many types:

- n-channel and p-channel (analog to npn/pnp for BJTs)

BJTs control the current flow (CE) via the base current. Field Effect transistors control the flow via the presence of an **electric field**. You have to apply a voltage, but (essentially) no current flows.

Many types:

- n-channel and p-channel (analog to npn/pnp for BJTs)
- Metal-Oxid-Semiconductor (MOSFET) or Junction FETs (JFET)

BJTs control the current flow (CE) via the base current. Field Effect transistors control the flow via the presence of an **electric field**. You have to apply a voltage, but (essentially) no current flows.

Many types:

- n-channel and p-channel (analog to npn/pnp for BJTs)
- Metal-Oxid-Semiconductor (MOSFET) or Junction FETs (JFET)
- Depletion or Enhancement mode

BJTs control the current flow (CE) via the base current. Field Effect transistors control the flow via the presence of an **electric field**. You have to apply a voltage, but (essentially) no current flows.



Many types:

- n-channel and p-channel (analog to npn/pnp for BJTs)
- Metal-Oxid-Semiconductor (MOSFET) or Junction FETs (JFET)
- Depletion or Enhancement mode



This gives 8 combinations, 5 are used, 4 are common: n/p-JFET dep. NMOS (enh/dep), PMOS(enh)

FET symbols

MOS

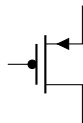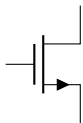



JFET

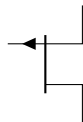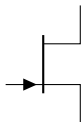

n-channel

p-channel

Nomenclature

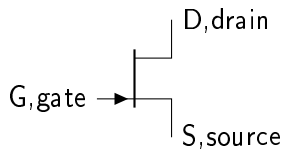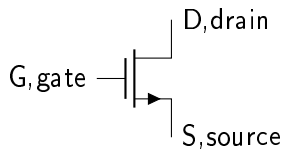


MOSFET (n-channel, enhancement)

Remember the definition of resistance: $R = l/A \times \rho$. A FET modifies the area A of the conductive part!

MOSFET (n-channel, enhancement)

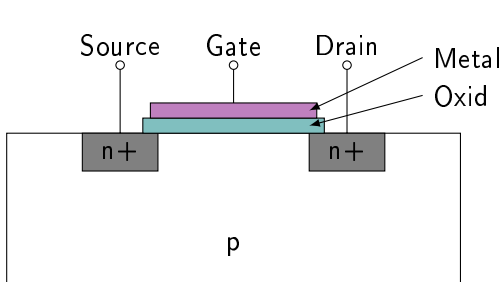
Remember the definition of resistance: $R = l/A \times \rho$. A FET modifies the area A of the conductive part!



- with $V_{GS} \leq 0$, no conductance

MOSFET (n-channel, enhancement)

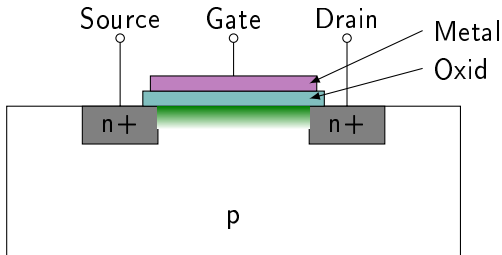
Remember the definition of resistance: $R = l/A \times \rho$. A FET modifies the area A of the conductive part!



- with $V_{GS} \leq 0$, no conductance
- with $V_{GS} > 0$, the holes close to the gate are repelled, a inverted region forms

MOSFET (n-channel, enhancement)

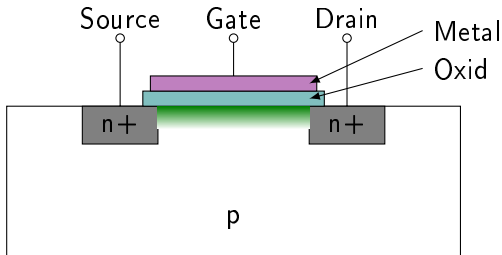Remember the definition of resistance: $R = l/A \times \rho$. A FET modifies the area A of the conductive part!



- with $V_{GS} \leq 0$, no conductance
 - with $V_{GS} > 0$, the holes close to the gate are repelled, an inverted region forms
 - A full channel forms for $V_{GS} > V_{threshold}$, a voltage V_{DS} can now drive a current.
- N.B: The D/S n and bulk p doped areas form a diode. It's important to keep this diode reverse biased. Often, the bulk is connected to the source, sometimes, it's available as a separate pin.

Operation modes: V_{GS} dependance

For an enhancement mode n-MOSFET, we have

- Cut-off region: $V_{GS} < V_{threshold}$, no current

Operation modes: V_{GS} dependance

For an enhancement mode n-MOSFET, we have

- Cut-off region: $V_{GS} < V_{threshold}$, no current
- For $V_{GS} > V_{threshold} = V_{th}$:
 - V_{DS} large ($V_{DS} > V_{GS} - V_{th}$): (current) saturation region = active region (different from BJT!)

$$I_D = \kappa(V_{GS} - V_{th})^2$$

Operation modes: V_{GS} dependance

For an enhancement mode n-MOSFET, we have

- Cut-off region: $V_{GS} < V_{threshold}$, no current
- For $V_{GS} > V_{threshold} = V_{th}$:
 - V_{DS} large ($V_{DS} > V_{GS} - V_{th}$): (current) saturation region = active region (different from BJT!)

$$I_D = \kappa(V_{GS} - V_{th})^2$$


- V_{DS} small: linear region

$$I_D = 2\kappa [(V_{GS} - V_{th})V_{DS} - V_{DS}^2/2]$$

Can interpret this as a voltage controlled resistor (but not quite ohmic)

$$R_{DS} \approx \frac{1}{2\kappa(V_{GS} - V_{th})}$$

Operation modes: V_{DS}

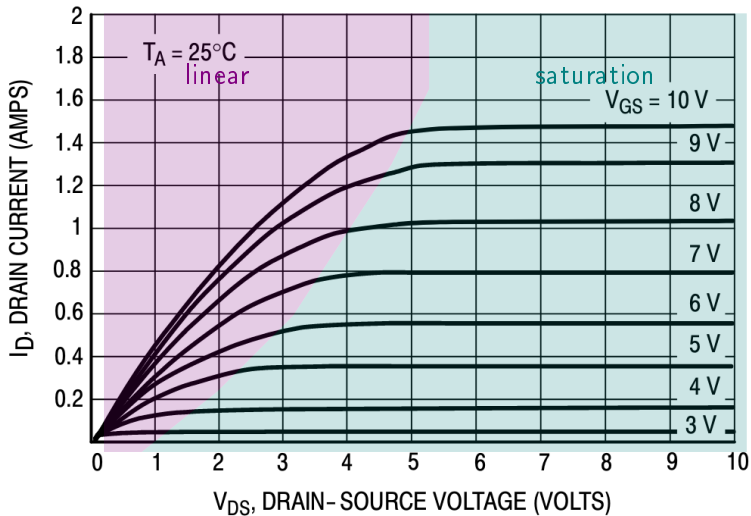


- One can dope the channel to manipulate V_{th}

- One can dope the channel to manipulate V_{th}
- One can even make V_{th} negative!


- One can dope the channel to manipulate V_{th}
- One can even make V_{th} negative!
 - there is current flow possible even at $V_{GS} = 0$
 - have to drive V_{GS} negative to stop flow.
 $V_{GS}(I_D = 0) = V_P$ "pinch-off voltage"
- Junction FETs can only be in depletion mode

Junction FET (n-channel)

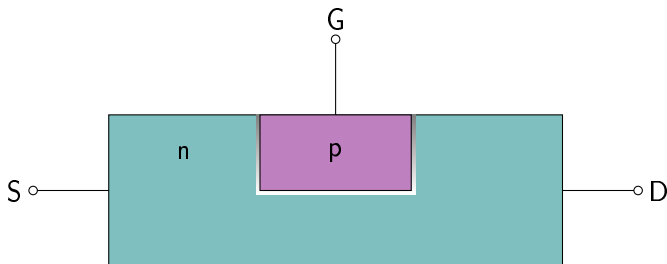


- $V_{GS} = 0$: Maximum channel width, maximum current, I_{DSS} (Drain current with gate Shorted to Source)
- NB: $V_{GS} > 0$ will quickly lead to large currents into the gate!

Junction FET (n-channel)

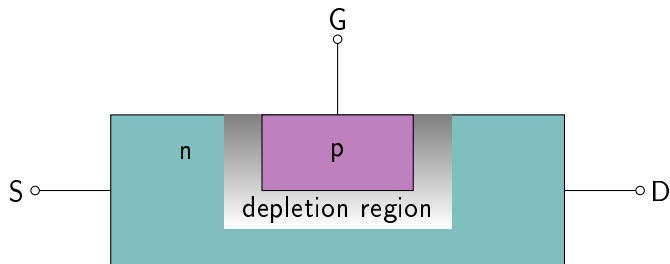

- $V_{GS} < 0$: Depletion region grows, makes channel smaller, $I_D < I_{DSS}$

Junction FET (n-channel)

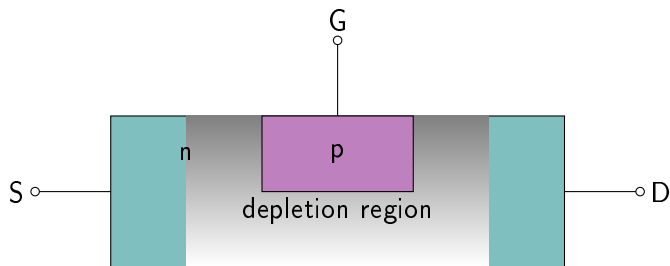

- $V_{GS} \leq V_P < 0$: Depletion region pinched off channel, $I_D \approx 0$

Advantages / Disadvantages of FET

Good:

- No current on the controlling side, only voltage required
- In other words: infinite input resistance.
- No static power draw on the controlling side, can achieve small $R(on)$ on the controlled side

Bad


- Easy to destroy with static electricity
- Device parameters have a bigger scattering. E.g V_{th} and V_p have often a spread of 1-5V between specimen!

- We can use the analog topologies of BJT
- Some circuits benefit greatly from FETs:
 - High-impedance/low current input: FETs need no current to operate, resistance in the order of $10^{14}\Omega$
 - Analog switches: see below
 - Digital logic: complementary MOS (pMOS and nMOS): no static power consumption
 - Power switching (MOSFET)
 - Linear circuits: Here, mostly JFET

Source follower


This is the equivalent of the emitter follower.

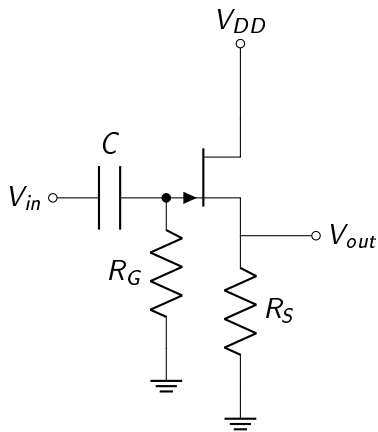- JFET: depletion mode:
conducting if $V_{GS} = 0$



Source follower

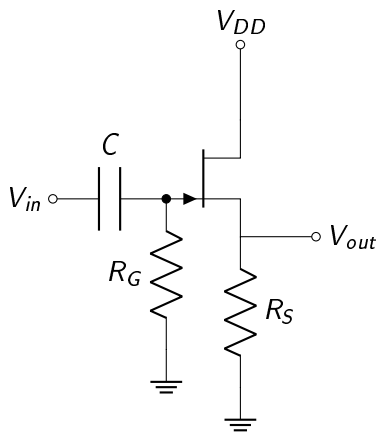
This is the equivalent of the emitter follower.



- JFET: depletion mode:
conducting if $V_{GS} = 0$
- R_G pulls G down to 0, so JFET
will start to conduct

Source follower

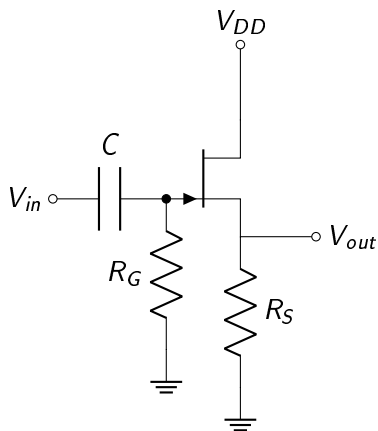
This is the equivalent of the emitter follower.



- JFET: depletion mode:
conducting if $V_{GS} = 0$
- R_G pulls G down to 0, so JFET will start to conduct
- That means that $V_S = I_D R_S$ increases, V_{GS} becomes negative

Source follower

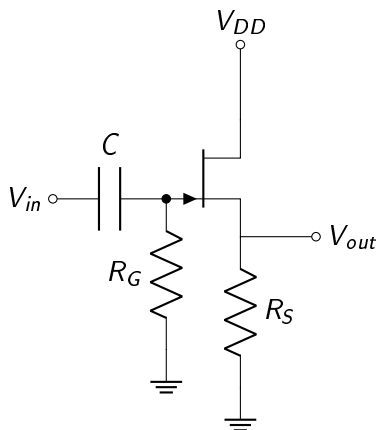
This is the equivalent of the emitter follower.



- JFET: depletion mode:
conducting if $V_{GS} = 0$
- R_G pulls G down to 0, so JFET will start to conduct
- That means that $V_S = I_D R_S$ increases, V_{GS} becomes negative
- Equilibrium = working point is reached, when
 $-V_{GS} = V_S = I_D(V_{GS})R_S$


Source follower

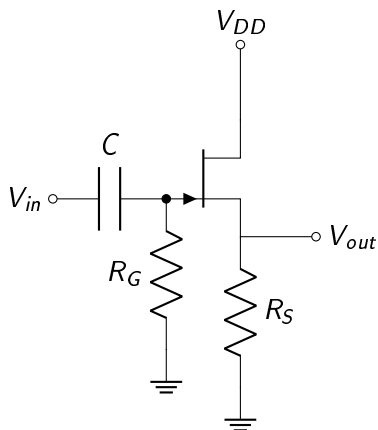This is the equivalent of the emitter follower.




- JFET: depletion mode:
conducting if $V_{GS} = 0$
- R_G pulls G down to 0, so JFET will start to conduct
- That means that $V_S = I_D R_S$ increases, V_{GS} becomes negative
- Equilibrium = working point is reached, when
$$-V_{GS} = V_S = I_D(V_{GS})R_S$$
- Input impedance is dominated by R_G , which can be MOhms

Analog switch

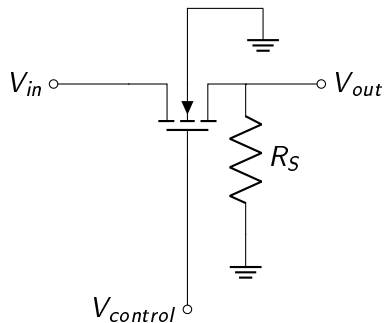


- Enhancement mode MOSFET

Analog switch

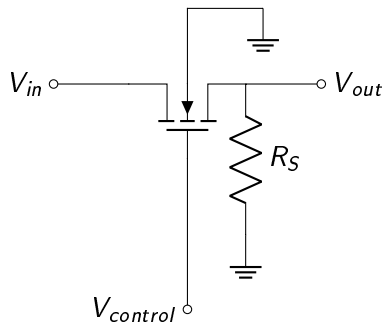


- Enhancement mode MOSFET
- Assume V_{in} is an analog signal > 0

Analog switch

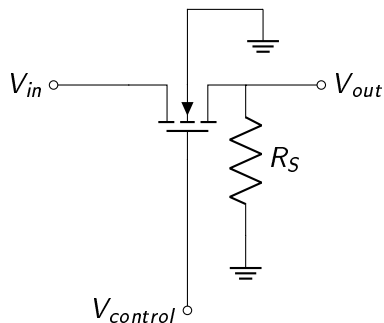


- Enhancement mode MOSFET
- Assume V_{in} is an analog signal > 0
- If $V_{control} \leq 0$, the MOSFET is not conducting, the output is 0

Analog switch

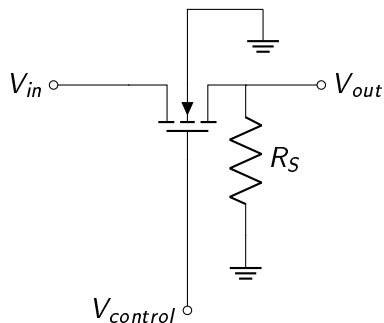

- Enhancement mode MOSFET
- Assume V_{in} is an analog signal > 0
- If $V_{control} \leq 0$, the MOSFET is not conducting, the output is 0
- if $V_{control} = V_{DD}$, all signals $0 < V_{in} < V_{DD}$ are passed through to V_{out}

Power switching

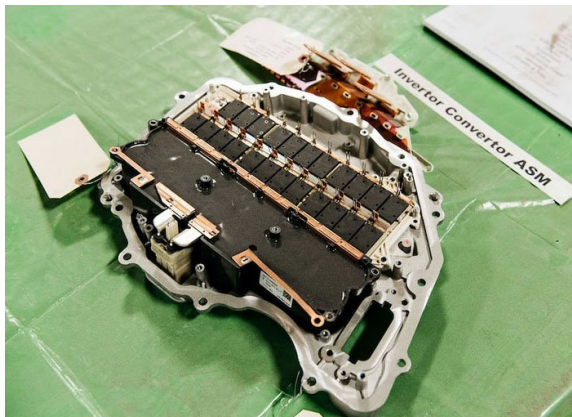


Model 3 inverter. Note two rows of rectangular devices

Taken from Motor Trend photos of Munro Ass. teardown

Each of the black devices can switch 100A at 650V....
24m Ω resistance when switched on

Logic: CMOS inverter

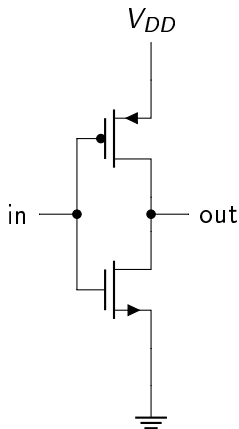

- A logic low input (0V) lets the upper FET conduct, which pulls the output to logic high (V_{DD})
- A logic high input (V_{DD}) lets the lower FET conduct, which pulls the output to logic low (0V)
- Ergo: $out = \bar{in}$